

# LC Tank with Resistance

Vikas Kurapati

*Roll No. : 130010058*

October 13, 2016

# Contents

### **Abstract**

The problem is to simulate the behaviour of a LC tank with a resistance applied across a voltage in series with given initial conditions of the charge in the capacitor and current in the inductor.